

Data Table
(a.k.a. “Not the results table”)
Kirchhoff’s Laws

Data for current values

Measured-(DMM) <i>Current ± δCurrent</i> (A)	Calculated (A)	% Difference
I ₁		
I ₂		
I ₃		

Data table for measured potentials

Loop1 Potentials $V \pm \delta V$ (V)	Loop2 Potentials $V \pm \delta V$ (V)	Loop3 Potentials $V \pm \delta V$ (V)
V _{fa}	V _{bc}	V _{fa}
V _{ab}	V _{cd}	V _{ab}
V _{be}	V _{de}	V _{bc}
V _{ef}	V _{eb}	V _{cd}
$\sum V_{loop} \pm \delta V_{loop}$	$\sum V_{loop} \pm \delta V_{loop}$	V _{de}
xxxxxxxxxxxxxxxxxxxxxxxx	xxxxxxxxxxxxxxxxxxxxxxxx	V _{ef}
xxxxxxxxxxxxxxxxxxxxxxxx	xxxxxxxxxxxxxxxxxxxxxxxx	$\sum V_{loop} \pm \delta V_{loop}$

Show minimum sample calculations (one each) for:

- 1) uncertainty in current, 2) uncertainty in voltage and 3) uncertainty in voltage sum.**